
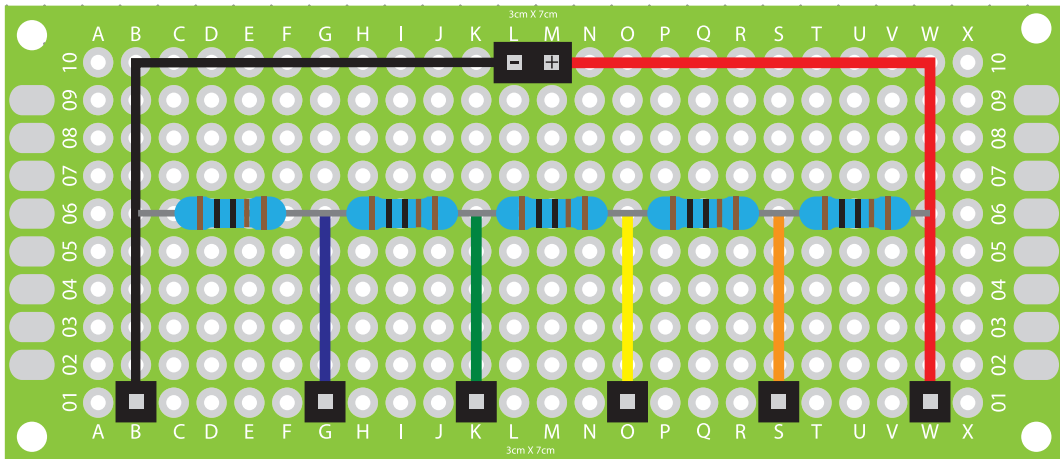



### Front View: Circuit Board Layout

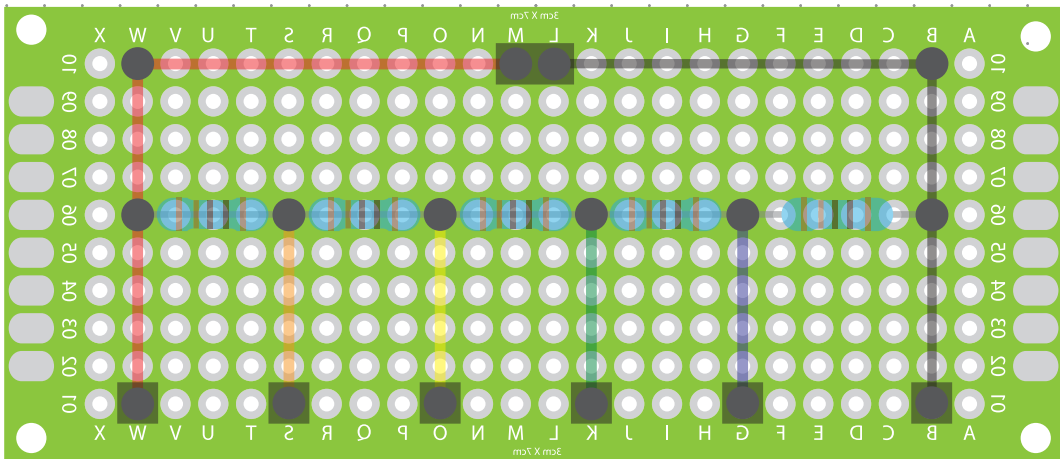

### Back View: Circuit Board Layout


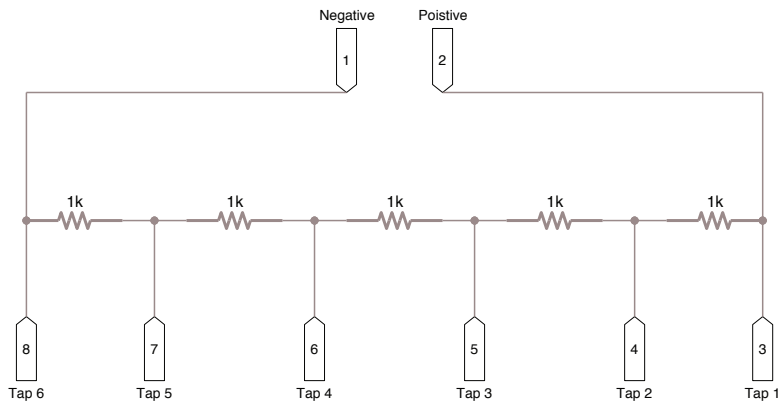
#### Electrical Schematics Resistor Tree Experiment



#### Materials:

- 1 3x7cm circuit board
- 5 1k resistor
- 8 Pin type bridge connector
- 1 15cm length of black wire
- 1 15cm length of red wire
- 1 5cm length of orange wire
- 1 5cm length of yellow wire
- 1 5cm length of green wire
- 1 5cm length of blue wire

Project: Resistor Tee Experiment

Client:

5mm Dot Grid

Designer: Scott A. Campbell

Builder:

Scale:

2:1