

Name:
Teacher:
Class:
Date:

Logic And Electrical Engineering - Practice Problems Set 1
逻辑和电子工程-练习题1

1. The diagram below shows part of a control circuit. At first both **input A** and **input B** are **low (0)**, and the lamp is **OFF**.
下图显示了控制电路的一部分。输入A和输入B均为低电平（0），指示灯灭。



- a) If **input A** becomes **high (1)**, the lamp will turn **ON**. Explain why this is.
如果输入A变为高电平（1），指示灯亮。解释这是为什么。
-
-
-
- b) If **input A** returns to a **low (0)** state after being in a **high (1)** state, the lamp will remain **ON**. Explain why this happens.
如果输入A在处于高（1）状态后返回低（0）状态，指示灯将保持亮。解释为什么会发生这种情况。
-
-
-
- c) What is a feedback loop?
什么是反馈电路？
-
-
-
- d) What effect does a negative feedback loop have on this control system?
负反馈电路对该控制系统有什么影响？
-
-
-

2. The names of four electrical devices are given on the left. What each device does is given on the right. Draw a line to join each device with what it does.
 左边是四个电气设备的名称，右边给是每个设备的功能。将每个设备与其对应功能连接起来。

LED	Measures current, voltage or resistance
Speaker	Emits light when a current flows through it
Multimeter	Produces an output sound
Microphone	Transfers sound energy to electrical energy

3. The following is a list of electrical components that may be used in electrical circuits 以下是电路中可能使用的电气部件列表：

capacitor(电容器) diode(二极管) microphone 麦克风) multimeter(万用表) transistor(晶体管)

- a) Allows current to flow in one direction only. 允许电流只向一个方向流动。

- b) Can store a small charge. 可以储存少量电荷。

- c) Can act as an electronic switch. 可以用作电子开关。

- d) Can be used to measure voltage. 可用于测量电压。

- e) Can act as a sound sensor .可以用作声音传感器。

4. The diagram following shows an input signal and an output signal. Which of the components listed in question 2 would result in this type of signal transformation?

下图显示了输入信号和输出信号。问题2中列出的哪些部件会导致这种类型的信号转换？

